

Capacitors

Capacitors 2 - connecting capacitors

Learning objectives

MUST (C)

Explain how the structure of a capacitor affects its properties

SHOULD (B)


Understand the derivation of the rule for finding total capacitances for capacitors in series/parallel

COULD (A/A*)

Calculate the capacitances of different capacitor combinations

STARTER: We know that the amount of charge that a capacitor can store is expressed by its **capacitance** (C). What physical features of a capacitor do you think affect its capacitance?

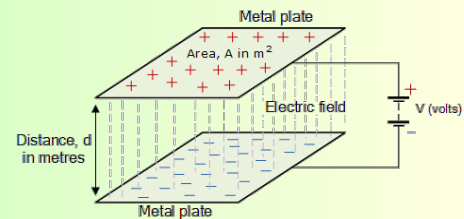EXTENSION: What factors do you think an equation to calculate capacitance would contain, and how would they relate (proportional, inverse...) to the capacitance?



$$C = \frac{\epsilon A}{d}$$

Where,

C = Capacitance in Farads

 ϵ = Permittivity of dielectric (absolute, not relative)

A = Area of plate overlap in square meters

d = Distance between plates in meters

Why is d inversely proportional to C?

Because the further apart the plates, the lower the electrostatic field between them.

Capacitors 1 homework: answers

1. C

2. C

3. D

4. A

5. D

6. B

7. D

8. B

Capacitors

Capacitors 2 - connecting capacitors

MUST (C)

Explain how the structure of a capacitor affects its properties

The equation for capacitance for a parallel plate capacitor with a vacuum between the plates is:

$$C = \frac{\epsilon_0 A}{d}$$

ϵ_0 is permittivity of free space, $8.854 \times 10^{-12} \text{ F m}^{-1}$

A is area of overlap, d is separation: convert units to m

When an insulator (or dielectric) other than a vacuum is used, the equation used is:

$$C = \frac{\epsilon A}{d} \quad \text{where} \quad \epsilon = \epsilon_r \epsilon_0 \quad \text{and} \quad \epsilon_r \text{ is } \mathbf{relative} \text{ permittivity.}$$


Material	ϵ_r
vacuum	1 (by definition)
air	1.0006
perspex	3.3
paper	4.0
mica	7.0
barium titanate	1200

ϵ is the permittivity for the insulator.



Two square completely overlapping plates with side length 1 cm, 2 mm apart, with a perspex dielectric.

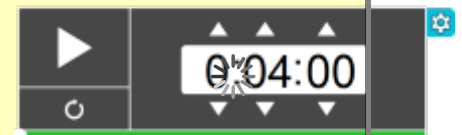What is the capacitance? ϵ_0 is $8.854 \times 10^{-12} \text{ F m}^{-1}$






Capacitance

Capacitors 2 - connecting capacitors

SHOULD (B)

Understand the derivation of the rule for finding total capacitances for capacitors in parallel/series

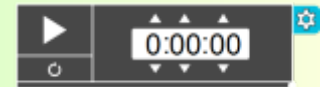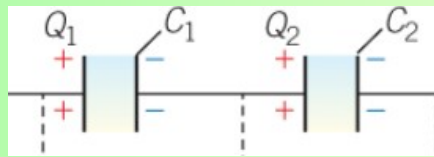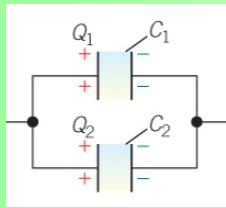Connecting capacitors in parallel and in series; will the overall capacitance increase or decrease?




Capacitors in parallel: the same V is across both capacitors.

Total charge $Q = Q_1 + Q_2$ (conservation of charge)

Recalling that $Q = CV$

If C is total capacitance, $CV = C_1V + C_2V$

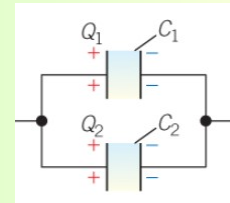V is the same in each case, so cancels out: $C = C_1 + C_2$



Total capacitance of capacitors in parallel = sum of the capacitances

Capacitors

Capacitors 2 - connecting capacitors


SHOULD (7)

Understand the derivation of the rule for finding total capacitances for capacitors in parallel/series

Capacitors in series

Potential difference split between the two capacitors.

Q is the same for all capacitors

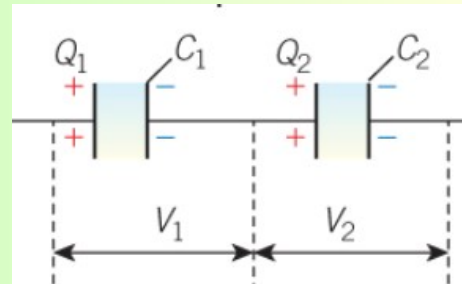Total p.d. $V = V_1 + V_2$ $V = Q/C$ $Q/C = Q/C_1 + Q/C_2$ Cancel out by Q throughout to give: $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$ 

Capacitors

Capacitors 2 - connecting capacitors

COULD (A/A*)


Calculate the capacitances of different capacitor combinations

Complete:

Summary questions 1-3 in section 21.2.

Summary questions 4-6 in section 21.2.

Key points:

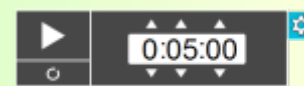Series: Q is constant, and $1/C = 1/C_1 + 1/C_2 \dots$ Parallel: V is constant, and $C = C_1 + C_2$ 

21.2

1 Parallel: $C = C_1 + C_2 = 100 + 100 = 200 \mu\text{F}$ [1]

Series: $C = (C_1^{-1} + C_2^{-1})^{-1} = (100^{-1} + 100^{-1})^{-1}$ [1]

$C = 50 \mu\text{F}$ [1]

The total capacitance for the parallel circuit is **twice** the capacitance of a single capacitor [1] and the total capacitance for the series circuit is **half** the capacitance of a single capacitor. [1]

2 $C = (C_1^{-1} + C_2^{-1})^{-1} = (120^{-1} + 120^{-1})^{-1}$ [1]

$C = 60 \text{ nF}$ [1]

$Q = VC = 60 \times 10^{-9} \times 1.5$ [1]

$Q = 9.0 \times 10^{-8} \text{ C}$ [1]

3 Total capacitance of N identical $1000 \mu\text{F}$ capacitors in parallel $= N \times 1000 \mu\text{F}$ [1]

Therefore, $N \times 1000 \times 10^{-6} = 4000$ [1]

$N = 4 \times 10^6$ (4 million) in parallel [1]

4 $C_1 = (100^{-1} + 500^{-1})^{-1} = 83.3 \mu\text{F}$ [2]

$C_2 = (50^{-1} + 200^{-1})^{-1} = 40 \mu\text{F}$ [2]

Total capacitance $= C_1 + C_2 = 83.3 + 40 \approx 123 \mu\text{F}$ [1]

5 The charge stored by each is the same and the p.d. across the combination is 6.0 V . [1]

$V = \frac{Q}{C} \propto \frac{1}{C}$, hence the p.d. across the capacitor with capacitance $2C$ will be half the p.d. across the capacitor with capacitance C . [1]

Therefore, p.d. across $C = 4.0 \text{ V}$ [1] and the p.d. across $2C = 2.0 \text{ V}$. [1]

6 $\frac{1}{17} = \frac{1}{C} + \frac{1}{20}$ [1]

$\frac{1}{C} = \frac{1}{17} - \frac{1}{20}$ [1]

$C = 113 \text{ nF} \approx 110 \text{ nF}$ [1]

Capacitors		Capacitors 2 - connecting capacitors
Learning objectives	MUST (C)	Understand the derivation of the rule for finding total capacitances for capacitors in parallel
	SHOULD (B)	Understand the derivation of the rule for finding total capacitances for capacitors in series
	COULD (A/A*)	Calculate the capacitances of different capacitor combinations

PLENARY: Three capacitors are in series: $10\mu\text{F}$, $20\mu\text{F}$ and $40\mu\text{F}$. Which (if any) has the highest potential difference across it? Why?

EXTENSION: What do we know about the total capacitance? Answer without any calculation.

