



Capacitance		Charging capacitors
Learning objectives	<b>MUST (C)</b>	Describe how current, p.d. and charge vary in a charging capacitor
	<b>SHOULD (B)</b>	Solve the exponential charging equation for all variables
	<b>COULD (A/A*)</b>	Apply all capacitor equations to solve exam-style questions

**STARTER:** In a thrilling episode of unmissable\* 1980s US drama 'Quincy ME', our hero used an extension cable as a defibrillator. You are a TV physics consultant; watch this footage and comment on any aspects of the physics involved. What is realistic? What is unrealistic? Could they have done it better?

\*for fans of weak plots and dodgy acting

Quincy ME





Capacitance	Charging capacitors
<b>MUST (C)</b>	Describe qualitatively how and why current, p.d. and charge vary in a charging capacitor
<b>SHOULD (B)</b>	Express I, V and Q quantitatively with respect to time

Recall from last lesson:

The capacitor to the right is uncharged. When the switch is closed, how will the following change?

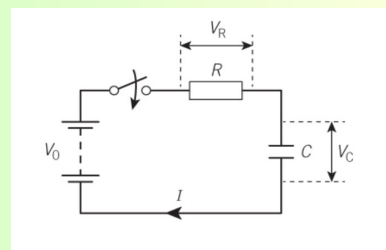- Current in the circuit
- $V_C$
- $V_R$
- Q for the capacitor



Potential difference

Charge


Current

--	--	--

$V_R$

--



Capacitance	Charging capacitors
<b>COULD (A/A*)</b>	Apply all capacitor equations to exam-style questions
<p>1) Summary questions: page 421</p> <p>2) Try practice questions 1 and 3 on page 424</p>	
<div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> <p><b>21.5</b></p> <ol style="list-style-type: none"> <li>The time constant of the circuit is very small because of the small resistance of the copper wires. Therefore the capacitor charges up in a very short time. [1]</li> <li>The current in the circuit and the p.d. across the resistor will both decrease exponentially with respect to time.</li> <li>Start the stopwatch when the switch is closed. Stop the stopwatch when the voltmeter reading has dropped to 37% of its initial reading of <math>V_0</math>. [1] The time recorded on the stopwatch is equal to the time constant. [1]</li> </ol> </div> <div style="width: 50%; text-align: right;">  </div> </div> <div style="margin-top: 20px;"> <p>4 <math>V_c = V_0 \left(1 - e^{-\frac{t}{CR}}\right) = 3.0 \times \left(1 - e^{-\frac{CR}{CR}}\right) = 3.0 \times 0.63</math> [1]  <math>V_c = 1.896 \text{ V} \approx 1.9 \text{ V}</math> [1]</p> <p>5 <math>CR = 120 \times 10^{-6} \times 1.0 \times 10^6 = 120 \text{ s}</math> [1]  <math>V_c = V_0 \left(1 - e^{-\frac{t}{CR}}\right) = 3.0 \times \left(1 - e^{-\frac{180}{120}}\right) = 3.0 \times 0.78</math> [1]  <math>V_c = 2.33 \text{ V} \approx 2.3 \text{ V}</math> [1]</p> <p>6 <math>V_c = V_R</math>, therefore <math>V_0 \left(1 - e^{-\frac{t}{CR}}\right) = V_0 e^{-\frac{t}{CR}}</math> [1]  <math>\frac{1}{2} = e^{-\frac{t}{CR}}</math> [1]  <math>\ln(0.5) = -\frac{t}{CR}</math> [1]  <math>t = 0.69CR</math> [1]</p> </div>	

